Homework #01


CMOS Course


Fundación Fulgor, Michel Saenz & Santiago Castro.

Deadline: June 19, 2026

Please complete the following tasks:

- Sketch and explain the **Current-Voltage (I/V) Characteristics** specifically for a **PMOS** transistor. Make sure to define the terminal voltages and how the current equations differ from the NMOS device in the triode, saturation regions.....
- Provide a comprehensive summary of the following second-order effects in MOS transistors. For each effect, include the **physical phenomenon** (what happens inside the silicon), the **electrical impact**, and the **mathematical representation**.
- Determine the region of operation of M1in each of the circuits show.

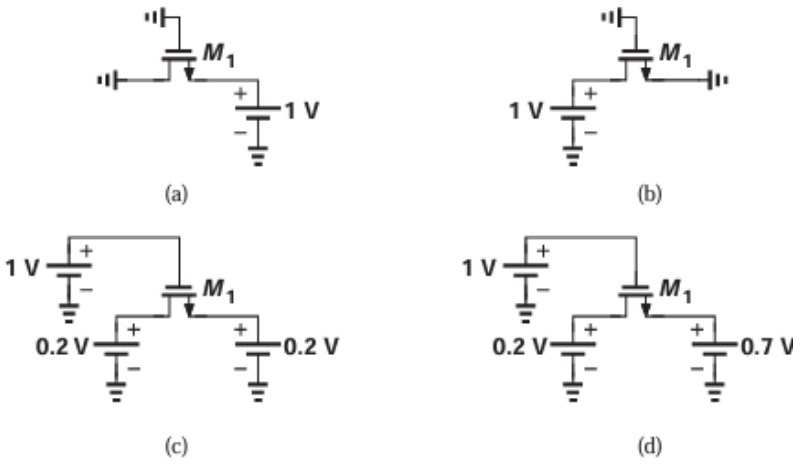

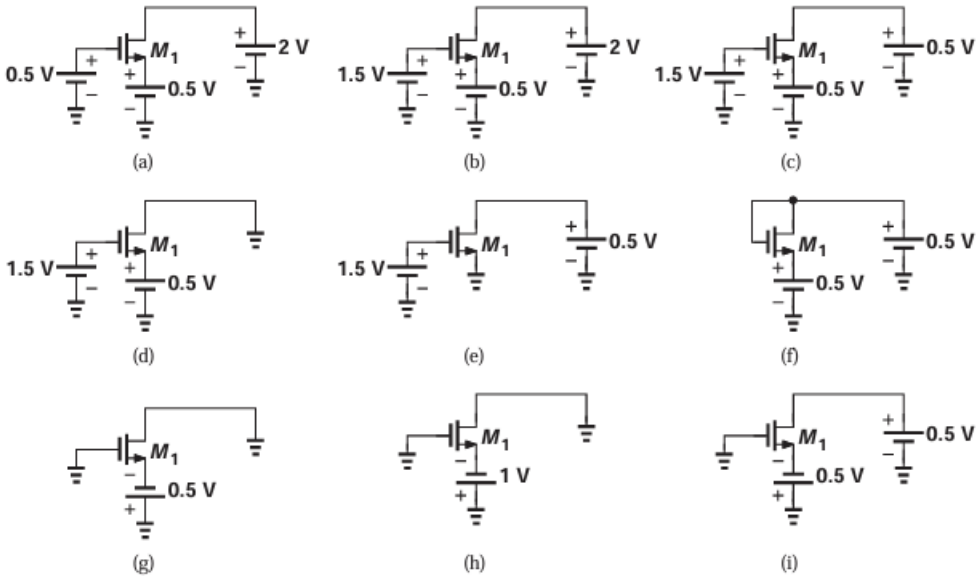

Submission Guidelines:

Format**:** You must export or scan your final solution into a single **PDF format**.

Platform: Upload the PDF file directly to our **Google Classroom** assignment slot before the deadline.