For the amplifier shown in Fig.1, asume that all transistors opérate in the saturation region and asume lambda=0. Determine the differential voltage gain of the circuit. Aditionally assume that R1=R2 and R3=R4.

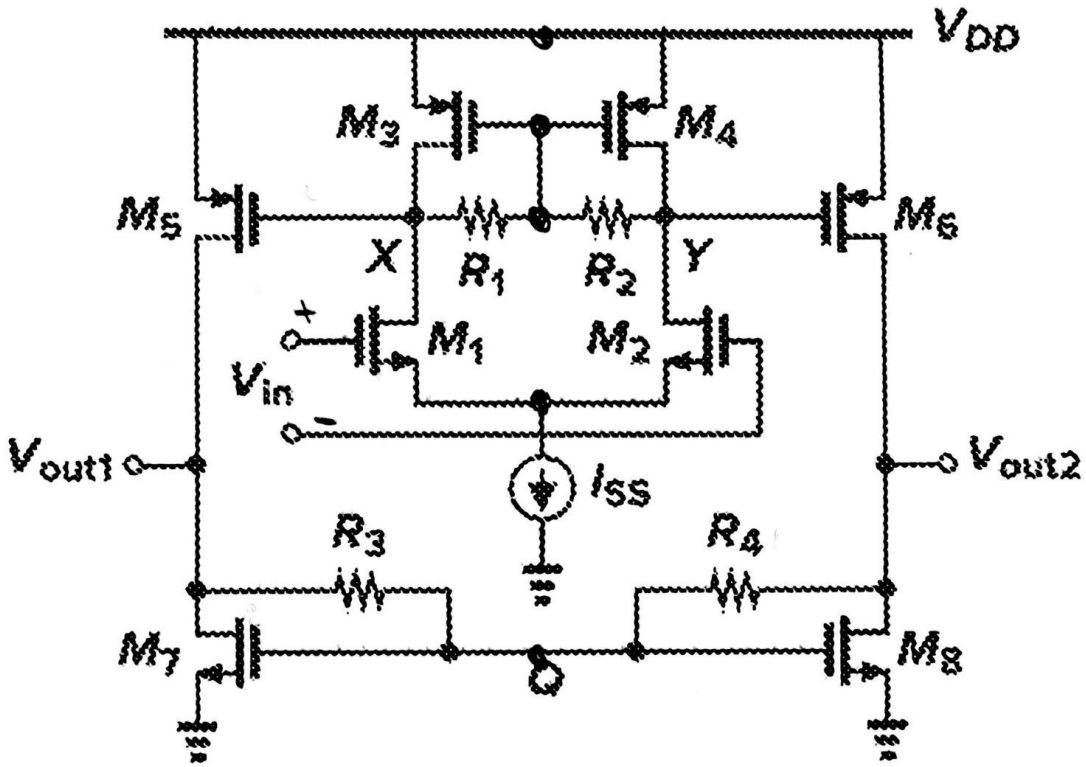



**Fig 1.**